



**The American
University in Cairo**

**School of Sciences
and Engineering**

Digital Design II

Project 1 Milestone 2 Report

Spring 2022

Dr. Cherif Salama

Abdelrahman Said – 900192935

Mohamed Farag – 900193654

Mostafa Ibrahim – 900192397

Contents

Contributions	3
Cell Heights	3
Determining t_{pdf} and t_{pdr}	3
Cell Design	3
Schematic Design	4
Layout Design	4
Simulation Schematic	4
Inverter	5
Stick Diagram	5
Inverter {size 1}	6
Inverter {size 2}	7
Inverter {size 4}	8
3 input NAND	9
Stick Diagram	9
NAND {size 1}	10
NAND {size 2}	11
3 input NOR	12
Stick Diagram	12
NOR {size 1}	13
NOR {size 2}	14
AOI22	15
Stick Diagram	15
AOI22 {size 1}	16
AOI22 {size 2}	18
Cell 5	20
Stick Diagram	20
Cell 5 {size 1} - $f(x,y,z,w) = (x+y+wz)'$	21
Cell 5 {size 2} - $f(x,y,z,w) = (x+y+wz)'$	22
Cell 6	23
Stick Diagram	23
Cell 6 {size 1} - $g(x,y,z) = [(x+y)(x+z)(y+z)]'$	24
Cell 6 {size 2} - $g(x,y,z) = [(x+y)(x+z)(y+z)]'$	26
Cell 7	28
Stick Diagram	28
Cell 7 {size 1} - $h(x,y,z,w) = [xz+(x+y+z)w]'$	29
Cell 7 {size 2} - $h(x,y,z,w) = [xz+(x+y+z)w]'$	31
List of Tables	33

Contributions

All group members worked together to be able to obtain consistent results. However, the responsibilities were divided as follows:

Mohammed Farag: NOT, NAND, NOR

Mostafa Ibrahim: AOI22, Cell 5

Abdulrahman Said: Cell 6 and 7

Cell Heights

To determine the cell heights, we first drew a stick diagram that was optimized using Euler's path, we calculated estimates of the heights based on the DRC rules provided, then, we implemented the layout on Electric VLSI. To determine the minimum cell height we abided by the rules that specify the dimensions of the components and the distances between them. Then, we designed the largest cell, determined its height, and designed the rest of the cells accordingly. In addition, we designed the layouts to have widths that were multiples of 4λ and that were the smallest possible.

The **standard cell height** that was used for all the cells was the height of **cell 7 size 2** which turned out to be **300λ** . The estimated cell height for cell 7 of size 2 was 292λ ; however, due to some constraints in the layout designing process.

Determining t_{pdf} and t_{pdr}

To determine t_{pdf} and t_{pdr} for each cell with the different loads, we connect the circuit with an inverter - size 1 for C_{inv} , size 2 for $2C_{inv}$, and size 4 for $4C_{inv}$ - then we indicate the transition time in the spice deck and we simulate.

Cell Design

Each required component had a schematic design, layout design, and simulation schematic. Size 1 and 2 of each cell were grouped in separated cell groups.

Schematic Design

For each cell we had to create two schematics one of size 1 and the other of size 2. The only difference between both schematics is that the transistors were sized accordingly. In our library, the exported inputs in the library were named A, B, C, D and the output was exported as OUT. The power and the ground were exported as VDD and GND respectively.

Layout Design


The layouts were designed according to the stick diagrams that we drew. In a size 2 cell we just multiply the size of the size 1 diffusion areas by 2. Eventually, all the cells were modified to have the cell height of the largest cell which is cell 7. The width of each cell was tailored to be a multiple of 4λ in all cells.

Simulation Schematic

In order to simulate the cells, we made a simulation schematic for each cell where we drag the icon of the cell to be simulated in it and connect it to inverters of size 1, 2, 4 in order to simulate the load capacitance of C_{inv} , $2C_{inv}$, $4C_{inv}$ respectively. After that, we write spice code that includes a pulsating input which controls the output of the cell. Then we measure the T_{pdf} and T_{pdf} . We run the simulation and get the values of the delays from the log of the simulation.

Inverter

Stick Diagram

 



To calculate the inverter cell Height: GND wire height + Minimum Distance Between 2 metals + (Diffusion Area $W_{min} \times nmos$ transistor size) + Minimum Distance Between 2 diffusion areas + (Diffusion Area $W_{min} \times pmos$ transistor size) + VDD wire height + Minimum Distance Between 2 metals.

- Height (size 1) = 60λ
- Height (size 2) = 92λ
- Height (size 4) = 156λ

Actual cell size used = 300λ



Inverter {size 1}

Layout & Schematic:

  



Inverter {size 2}

Layout & Schematic:

  


Inverter {size 4}

Layout & Schematic:

  

3 input NAND

Stick Diagram

 

Cell height = GND wire height + Minimum Distance Between 2 metals + (Diffusion Area $W_{min} \times nmos$ transistor size) + Minimum Distance Between 2 diffusion areas + (Diffusion Area $W_{min} \times pmos$ transistor size) + Minimum Distance Between 2 metals + VDD wire height.



Height (size 1) = $4 + 4 + 4 \times 3 + 12 + 4 \times 7 + 4 + 4 = 68\lambda$

Height (size 2) = $4 + 4 + 4 \times (2 \times 3) + 12 + 4 \times (2 \times 7) + 4 + 4 + 4 + 4 = 116\lambda$

Actual Size Used = 300λ



NAND {size 1}

Layout & Schematic:

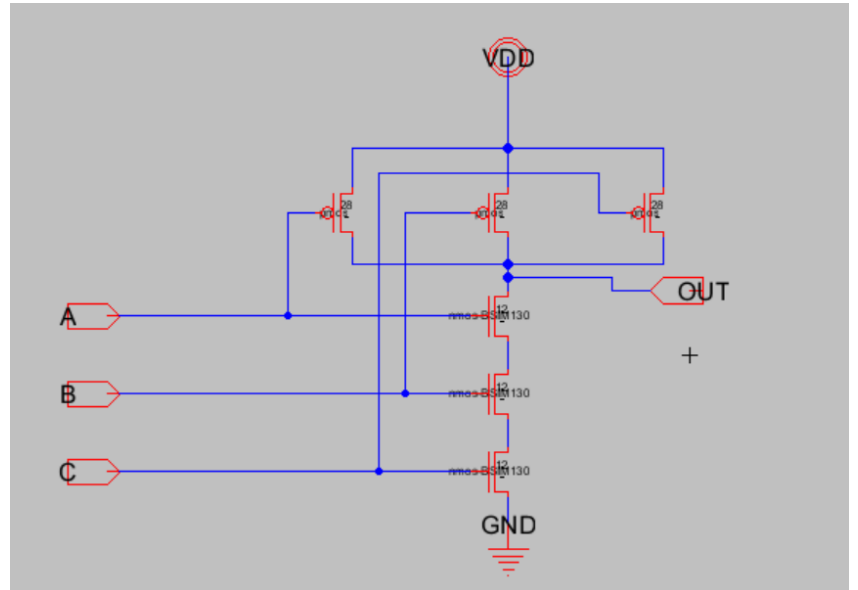 


NAND {size 2}

Layout & Schematic:

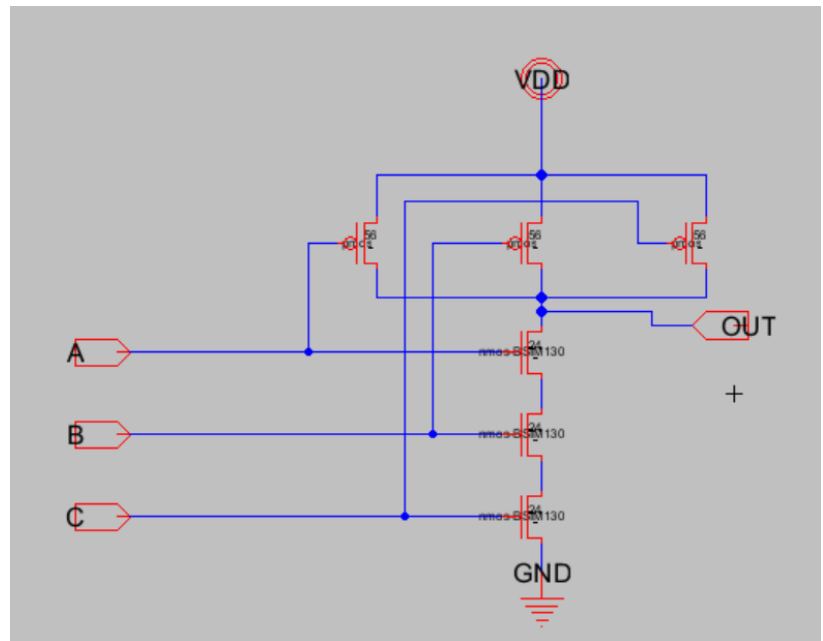 

3 input NOR

Stick Diagram


 


Height (size 1) = 116λ

Height (size 2) = 204λ



NOR {size 1}

Layout & Schematic:

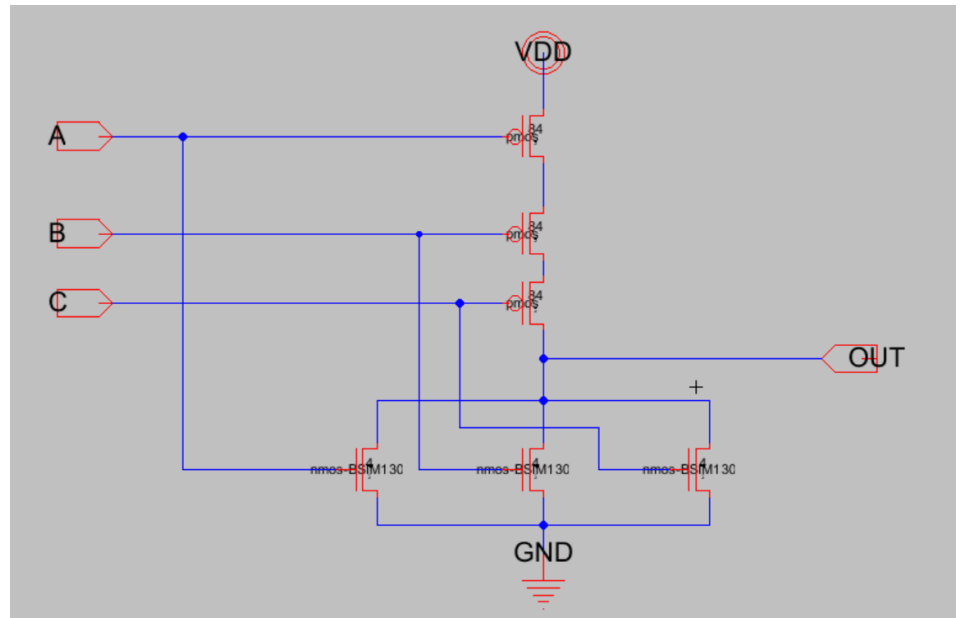 


NOR {size 2}

Layout & Schematic:

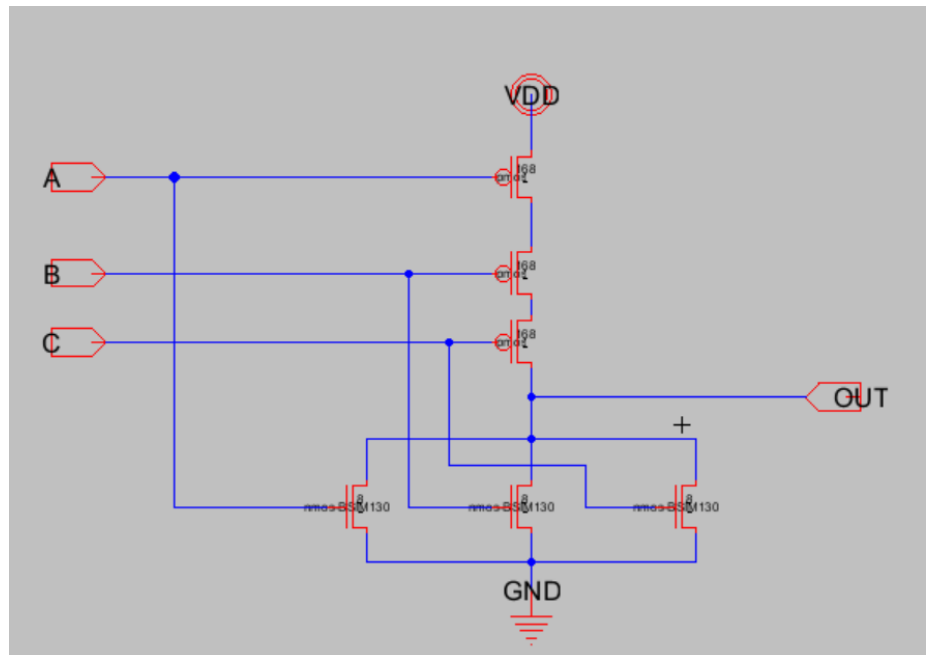 

AOI22

Stick Diagram

 


Height (size 1) = 108λ


Height (size 2) = 172λ

AOI22 {size 1}

Layout:

 


Schematic:

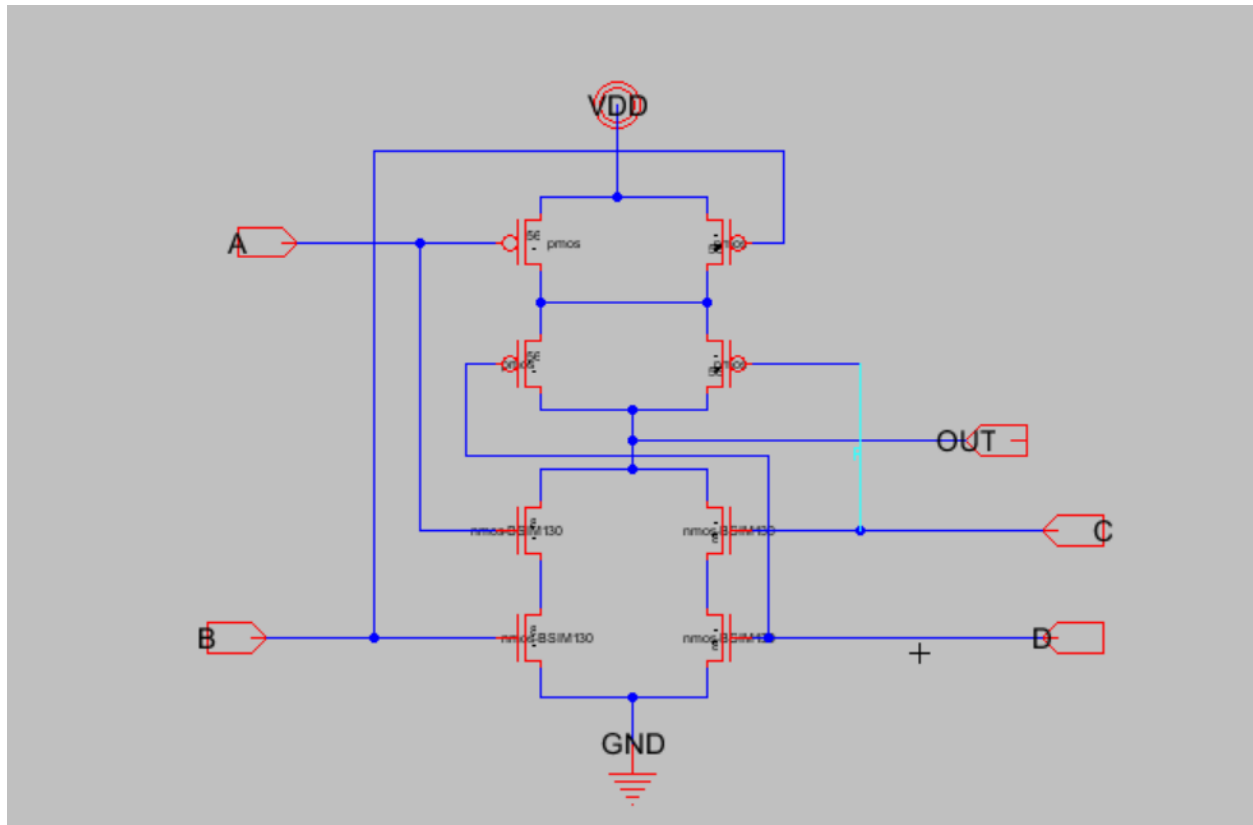


AOI22 {size 2}

Layout:

 


Schematic:

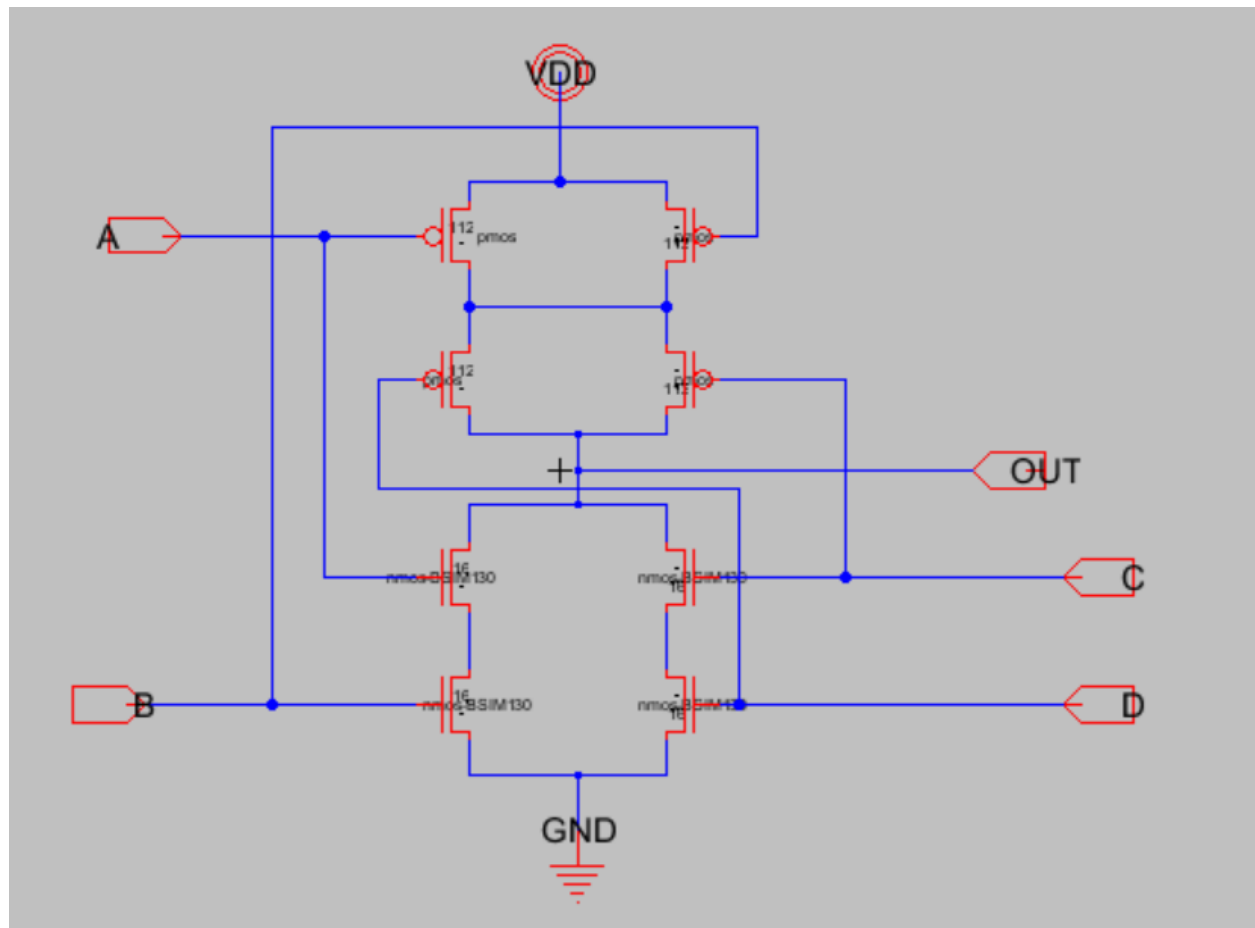

Cell 5

Stick Diagram

$$f(x,y,z,w) = (x+y+wz)'$$

 


Height (size 1) = 136λ


Height (size 2) = 228λ

Cell 5 {size 1} - $f(x,y,z,w) = (x+y+wz)'$

Layout:

 


Schematic:

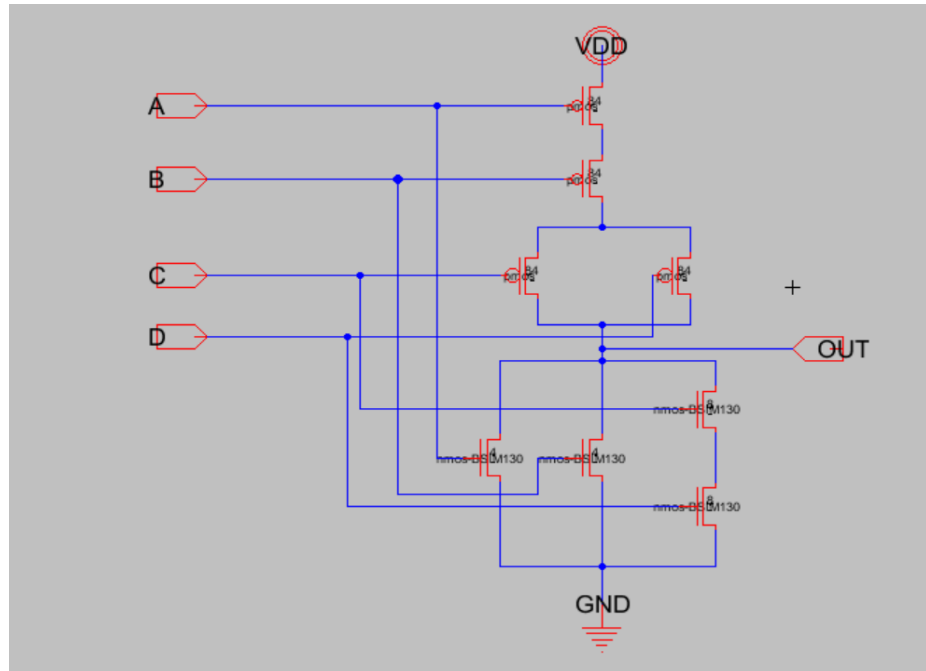


Cell 5 {size 2} - $f(x,y,z,w) = (x+y+wz)'$

Layout:

 


Schematic:

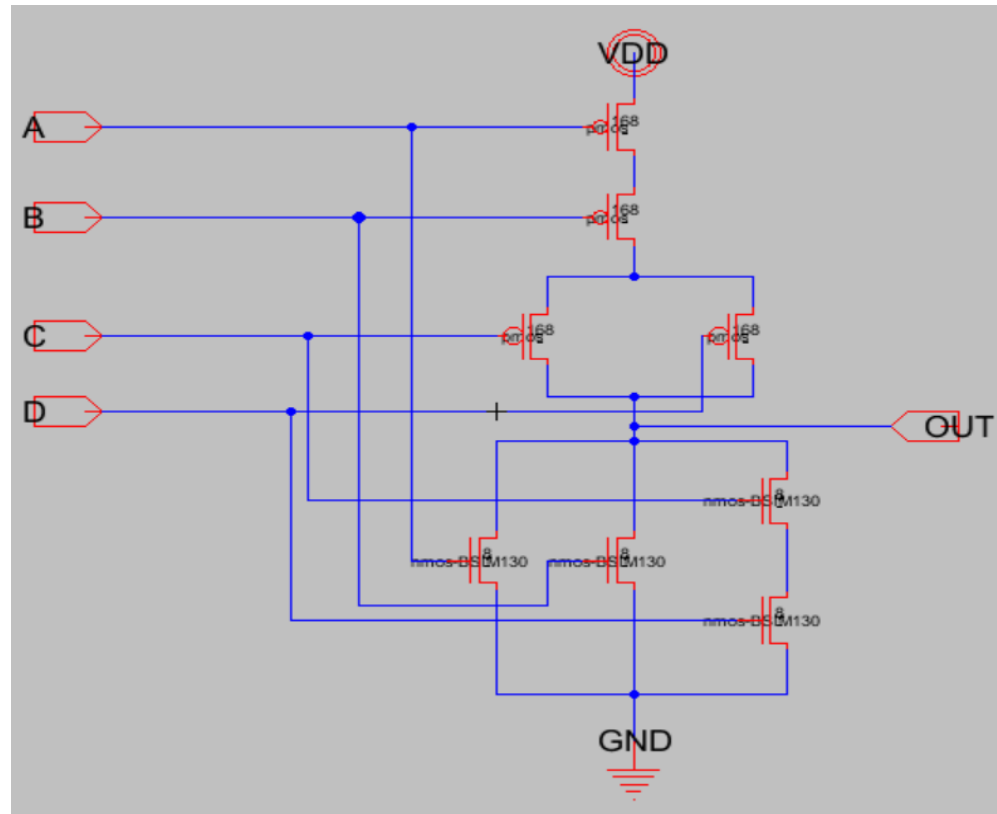

Cell 6

Stick Diagram

$$g(x,y,z) = [(x+y)(x+z)(y+z)]'$$

 


Height (size 1) = 128λ


Height (size 2) = 196λ

Cell 6 {size 1} - $g(x,y,z) = [(x+y)(x+z)(y+z)]'$

Layout:

 


Schematic

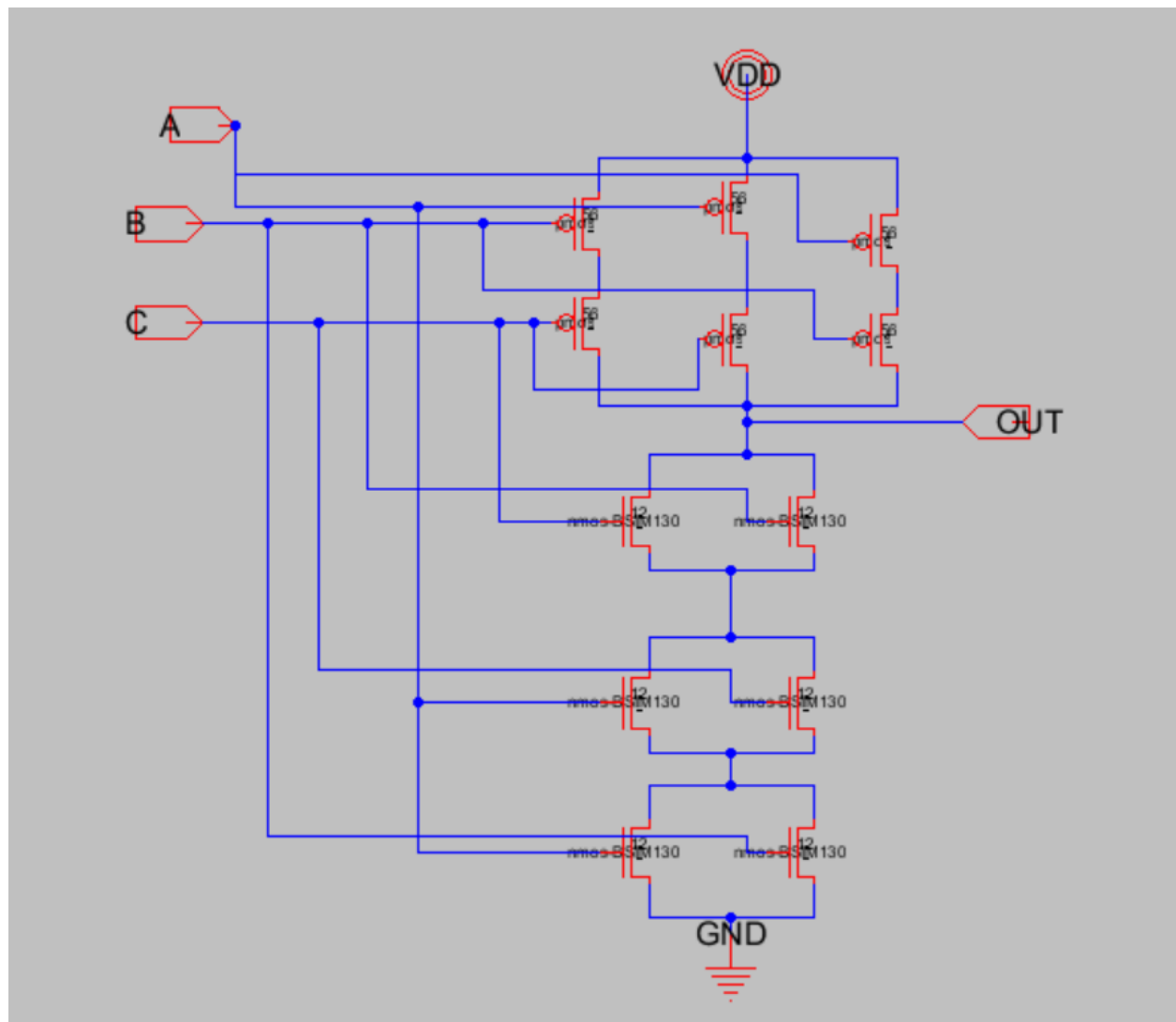


Cell 6 {size 2} - $g(x,y,z) = [(x+y)(x+z)(y+z)]'$

Layout:

 


Schematic:

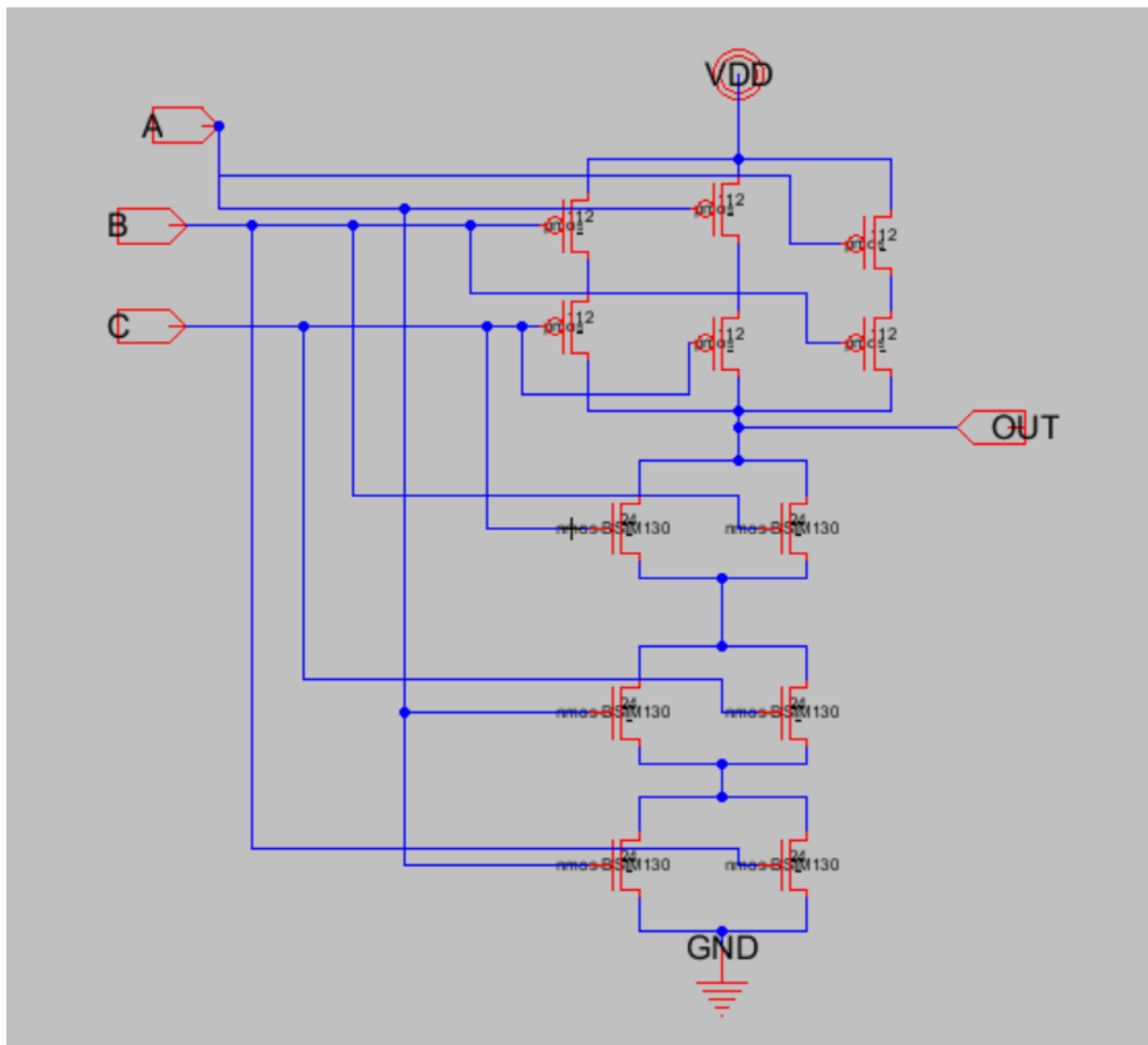

Cell 7

Stick Diagram

$$h(x,y,z,w) = [xz + (x+y+z)w]'$$

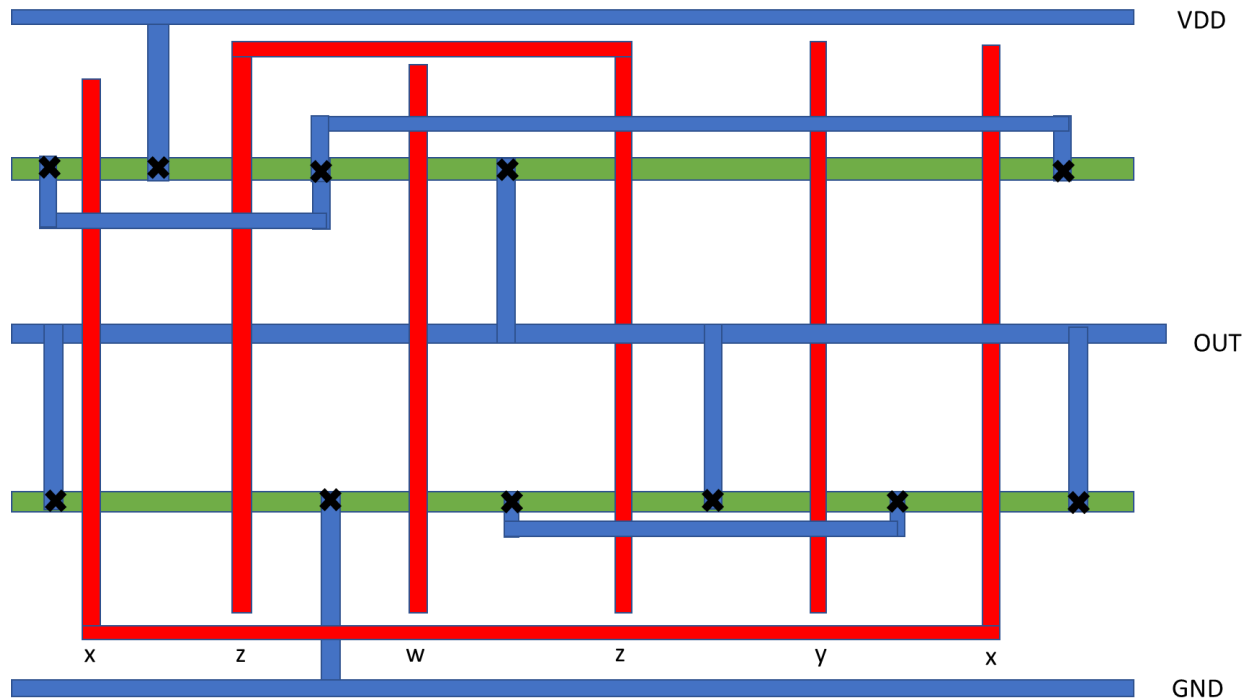


Height (size 1) = 172λ


Height (size 2) = 292λ

Cell 7 {size 1} - $h(x,y,z,w) = [xz+(x+y+z)w]'$

Layout:

 


Schematic:

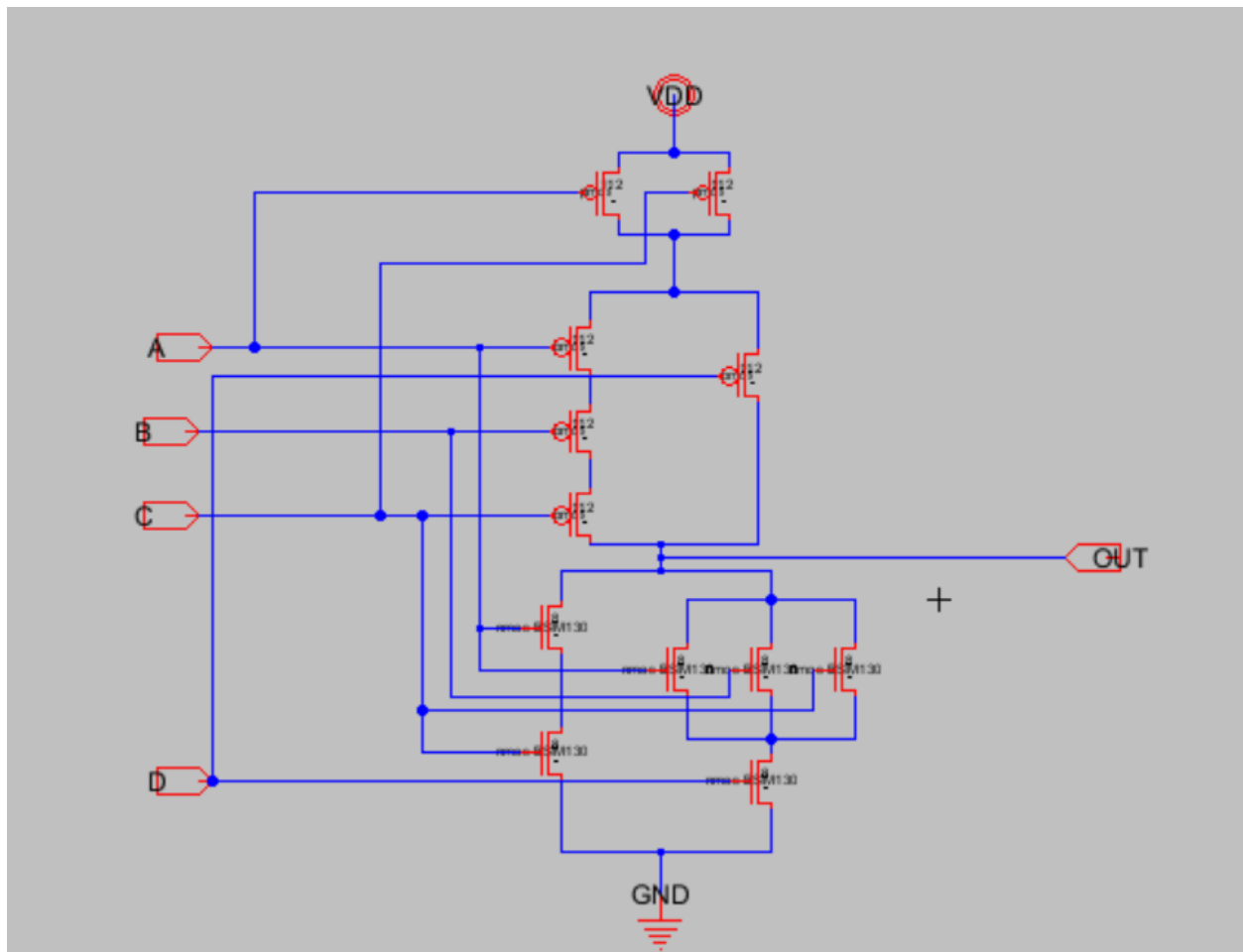


Cell 7 {size 2} - $h(x,y,z,w) = [xz+(x+y+z)w]$

Layout:

 

Schematic:

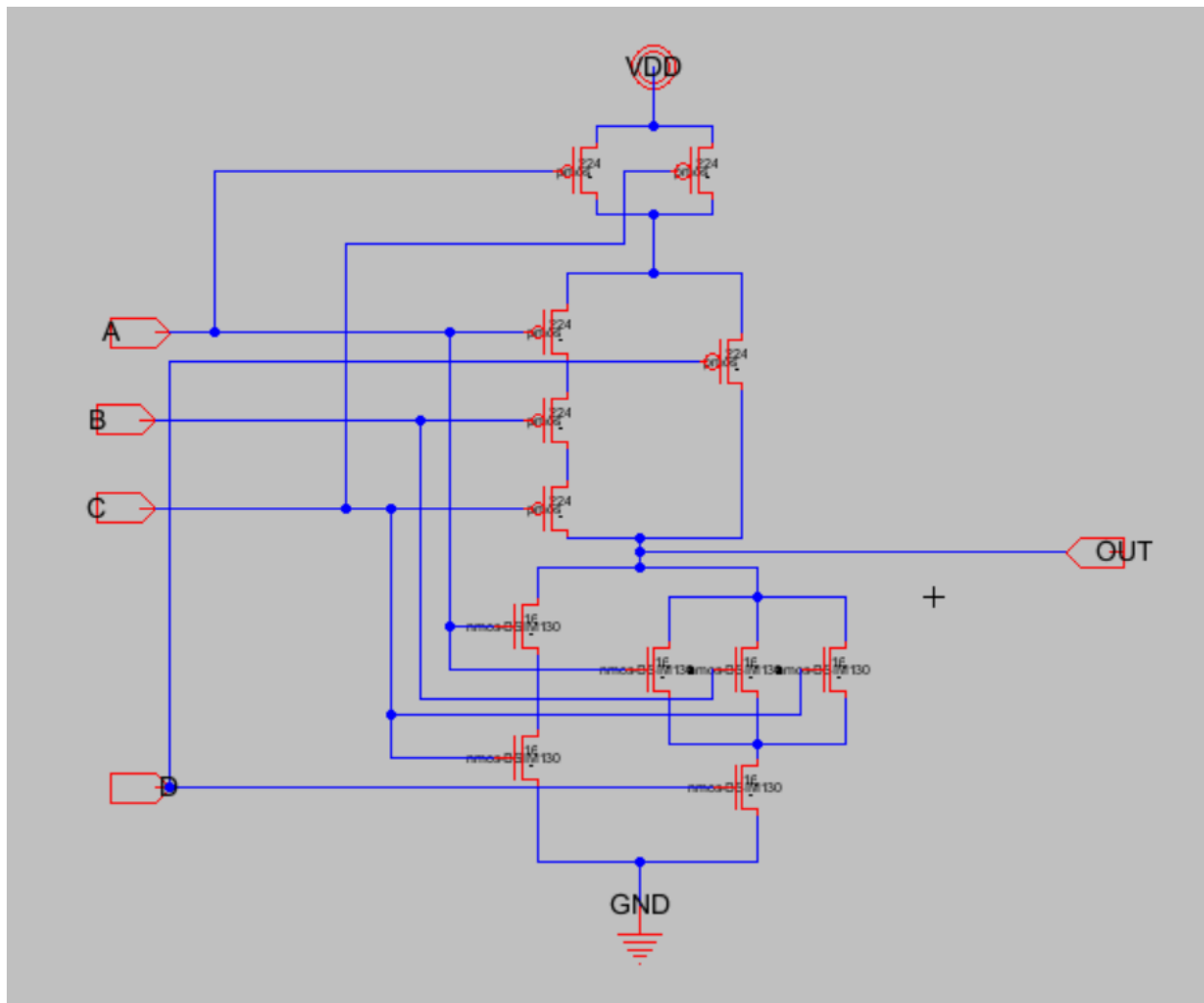

Size 1 Inverter T _{pdr}			
Transition/C _{inv}	C _{inv}	2C _{inv}	4C _{inv}
0ps	5.0040E-10	5.7047E-10	6.8223E-10
100ps	2.4357E-10	3.0002E-10	4.1281E-10
400ps	4.4045E-10	5.0360E-10	6.1389E-10

Size 1 Inverter T _{pdf}			
Transition/C _{inv}	C _{inv}	2C _{inv}	4C _{inv}
0ps	6.0197E-09	6.0777E-09	6.1777E-09
125ps	5.3598E-09	5.4144E-09	5.5182E-09
500ps	5.8559E-09	5.9096E-09	6.0107E-09

Size 2 Inverter T _{pdr}			
Transition/C _{inv}	C _{inv}	2C _{inv}	4C _{inv}
0ps	4.5668E-10	5.0065E-10	5.7049E-10
125ps	2.1632E-10	2.4396E-10	3.0024E-10
500ps	3.9945E-10	4.4069E-10	5.0387E-10

Size 2 Inverter T _{pdf}			
Transition/C _{inv}	C _{inv}	2C _{inv}	4C _{inv}
0ps	5.9843E-09	6.0192E-09	6.0765E-09
125ps	5.3322E-09	5.3595E-09	5.4120E-09
500ps	5.8236E-09	5.8555E-09	5.9085E-10

Size 4 Inverter T _{pdr}			
Transition/C _{inv}	C _{inv}	2C _{inv}	4C _{inv}
0ps	4.3122E-10	4.5816E-10	5.0161E-10
125ps	2.0541E-10	2.1737E-10	2.4377E-10
500ps	3.7688E-10	4.0151E-10	4.4139E-10

Size 4 Inverter T _{pdf}			
Transition/C _{inv}	C _{inv}	2C _{inv}	4C _{inv}
0ps	5.9634E-09	5.985E-09	6.019E-09
125ps	5.3188E-09	5.332E-09	5.359E-09
500ps	5.8050E-09	5.824E-09	5.855E-09

Size 1 NAND T _{pdr}			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	5.8807E-10	6.4034E-10	7.5122E-10
125ps	3.1242E-10	3.6840E-10	4.8043E-10
500ps	5.1648E-10	5.7077E-10	6.8294E-10

Size 1 NAND T _{pdf}			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	5.9764E-09	6.0197E-09	6.1009E-09
125ps	5.3804E-09	5.4219E-09	5.5024E-09
500ps	5.8275E-09	5.8685E-09	5.9505E-09

Size 2 NAND T _{pdr}			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	5.5784E-10	5.8736E-10	6.4112E-10
125ps	2.8394E-10	3.1197E-10	3.6805E-10
500ps	4.9051E-10	5.1737E-10	5.7149E-10

Size 2 NAND T _{pdf}			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	5.9524E-09	5.9760E-09	6.0189E-10
125ps	5.3589E-09	5.3799E-09	5.4204E-09
500ps	5.8045E-09	5.8267E-09	5.8688E-09

Size 1 NOR T _{pdr}			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	4.89615E-10	5.5079E-10	6.5641E-10
125ps	2.54065E-10	3.0221E-10	4.0372E-10
500ps	4.34678E-10	4.9525E-10	5.9218E-10

Size 1 NOR T _{pdf}			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	6.1200E-09	6.1732E-09	6.2804E-09
125ps	5.4494E-09	5.5105E-09	5.6288E-10
500ps	5.9507E-09	6.0052E-09	6.1137E-10

Size 2 NOR T _{pdr}			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	4.5408E-10	4.9141E-10	5.5175E-10
125ps	2.3261E-10	2.5512E-10	3.0297E-10
500ps	4.0246E-10	4.3678E-10	4.9538E-10

Size 2 NOR T _{pdf}			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	6.0938E-09	6.1198E-09	6.1721E-09
125ps	5.4197E-09	5.4499E-09	5.5098E-09
500ps	5.9241E-09	5.9509E-09	6.0038E-09

Size 1 AOI22 Tpdf			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	5.90698E-10	5.7764E-10	7.4571E-10
125ps	3.36530E-10	3.8877E-10	4.9137E-10
500ps	5.26136E-10	6.4210E-10	6.8201E-10

Size 1 AOI22 Tpdf			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	6.18713E-09	6.11569E-09	6.44615E-09
125ps	5.56180E-09	5.65874E-09	5.84553E-09
500ps	6.02724E-09	6.27347E-10	6.29039E-10

Size 2 AOI22 Tpdf			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	5.6019E-10	5.2674E-10	6.4286E-10
125ps	3.1174E-10	3.3686E-10	3.8788E-10
500ps	5.0149E-10	5.9137E-10	5.7811E-10

Size 2 AOI22 Tpdf			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	6.14386E-09	6.02623E-09	6.27159E-09
125ps	5.51209E-09	5.56076E-09	5.65769E-09
500ps	5.98269E-09	6.18579E-09	6.11403E-09

Size 1 Cell 5 Tpdf				
Transition/Cinv	Cinv	2Cinv	4Cinv	
0ps	6.1437E-09	6.1906E-09	6.2808E-09	
125ps	5.5508E-09	5.6000E-09	5.6980E-09	
500ps	6.1437E-09	6.1906E-09	6.2808E-09	
Size 1 Cell 5 Tpdf				
Transition/Cinv	Cinv	2Cinv	4Cinv	
0ps	6.2498E-10	6.8378E-10	7.9650E-10	
125ps	3.8409E-10	4.4088E-10	5.5646E-10	
500ps	6.2498E-10	6.8378E-10	7.9650E-10	

Size 2 Cell 5 Tpdf				
Transition/Cinv	Cinv	2Cinv	4Cinv	
0ps	6.2595E-09	6.3080E-09	5.8192E-09	
125ps	5.6669E-09	5.7182E-09	5.8192E-09	
500ps	6.2595E-09	6.3080E-09	6.3991E-09	
Size 2 Cell 5 Tpdf				
Transition/Cinv	Cinv	2Cinv	4Cinv	
0ps	5.6395E-10	6.0418E-10	4.3131E-10	
125ps	3.5066E-10	3.7651E-10	4.3131E-10	
500ps	5.6395E-10	6.0418E-10	6.7024E-10	

Size 1 Cell 6 Tpdf			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	6.1891E-09	6.2273E-09	6.2983E-09
125ps	5.6286E-09	5.6655E-09	5.7374E-09
500ps	6.1891E-09	6.2273E-09	6.2983E-09
Size 1 Cell 6 Tpdf			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	7.2285E-10	7.8359E-10	9.0292E-10
125ps	5.1153E-10	5.6988E-10	6.9074E-10
500ps	7.2285E-10	7.8359E-10	9.0292E-10

Size 2 Cell 6 Tpdf				
	Transition/Cinv	Cinv	2Cinv	4Cinv
	0ps	6.1704E-09	6.1897E-09	6.2261E-09
	125ps	5.6098E-09	5.6282E-09	5.6659E-09
	500ps	6.1704E-09	6.1897E-09	6.2261E-09
Size 2 Cell 6 Tpdf				
	Transition/Cinv	Cinv	2Cinv	4Cinv
	0ps	6.9337E-10	7.2390E-10	7.8447E-10
	125ps	4.7975E-10	5.1219E-10	5.7285E-10
	500ps	6.9337E-10	7.2390E-10	7.8447E-10

Size 1 Cell 7 Tpdr			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	6.7036E-09	6.7355E-09	6.8179E-09
125ps	6.1683E-09	6.1994E-09	6.2832E-09
500ps	6.7036E-09	6.7355E-09	6.8179E-09
Size 1 Cell 7 Tpdf			
Transition/Cinv	Cinv	2Cinv	4Cinv
0ps	7.1355E-10	7.3838E-10	8.0397E-10
125ps	5.0319E-10	5.2498E-10	5.8730E-10
125ps	7.1355E-10	7.3838E-10	8.0397E-10

Size 2 Cell 7 Tpdr				
	Transition/Cinv	Cinv	2Cinv	4Cinv
	0ps	6.6778E-09	6.6851E-09	6.7229E-09
	100ps	6.1394E-09	6.1459E-09	6.1854E-09
	400ps	6.6778E-10	6.6851E-10	6.7229E-09
Size 2 Cell 7 Tpdf				
	Transition/Cinv	Cinv	2Cinv	4Cinv
	0ps	6.9616E-10	7.0209E-10	7.3463E-10
	100ps	4.8920E-10	4.9290E-10	5.2214E-10
	400ps	6.9616E-10	7.0209E-10	7.3463E-10